



Credit Hour System  
CMPN101



Cairo University  
Faculty of Engineering

Logic Project: Team 13

Team Members:

Name	ID
Hossam Eldeen Khaled AbdelGawad	1190182
Mohamed Hassan Jassim	1180614
Abdallah Gamal Abdelhady Ghita	4200380
Amr Mohmmmed Shams El_Dieen	


Work Distribution

Name	Operations
------	------------

Hossam Eldeen Khaled AbdelGawad	Multiply (4-Bit Adder,HA,FA)
Mohamed Hassan Jassim	And, Or, Xor, Shift Right, Shift Left
Abdallah Gamal Abdelhady Ghita	Move, Not, Main circuit
Amr Mohmmmed Shams El_Dieen	Add, Subtract , Negative

## Modules


### Move:

 
 
### Number of gates:


Total: There are Zero gates in this Operation

**How it was made:** We simply put the input operand 1 in the latter half of the output preceded by the Four ground cables. As in 0000XXXX



### Negative:

**Add:**

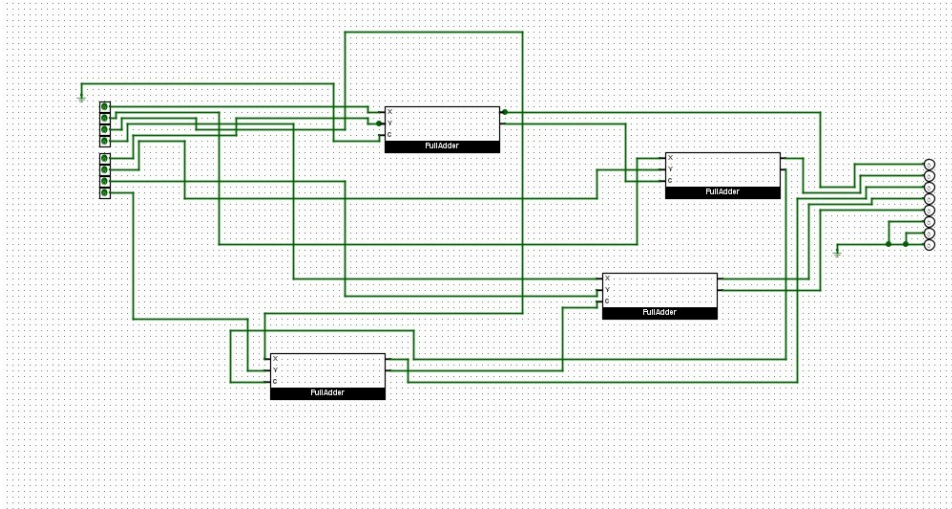

### Number of gates:


Total: 20

Detailed: 8 xor + 8 and + 4 or

### How it was made:

I used the full adder to add each bit in the two operand in a full adder and the carry goes into the next full adder

### Subtract:

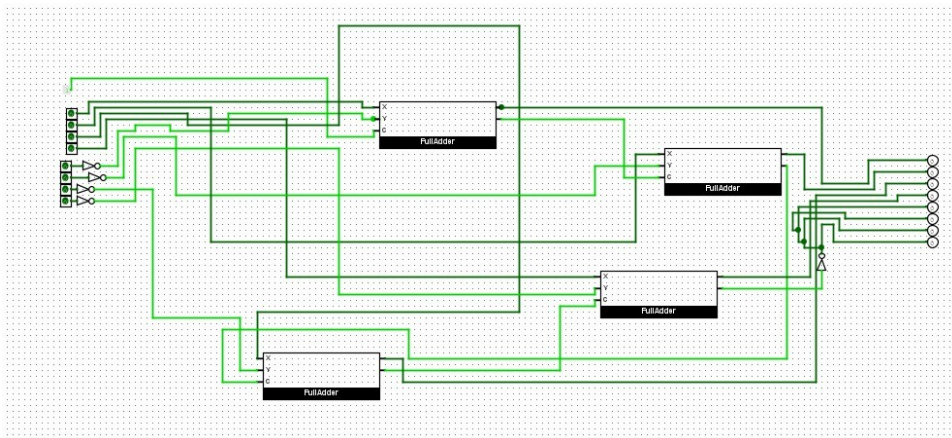


### Number of gates:

Total: 25


Detailed: 5 not + 8 xor + 8 and + 4 or

How it was made:

## Multiply:

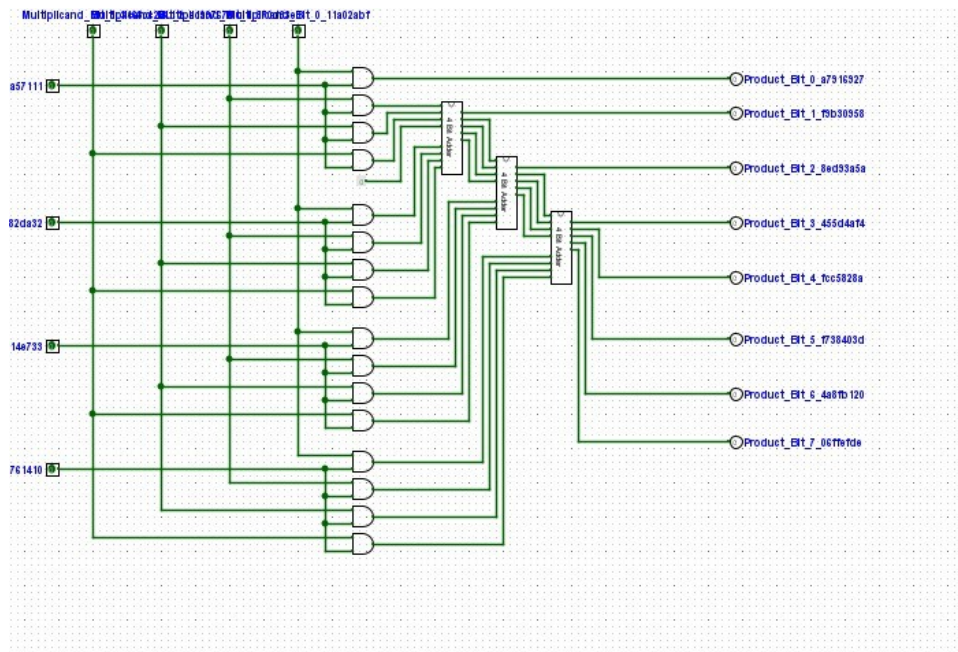

4 Bit Adder:

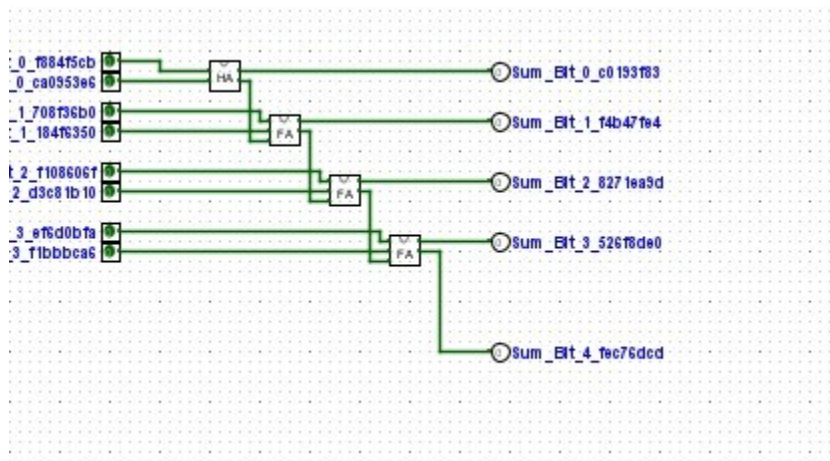


Number of gates:

Total=61

37 And + 21 Xor + 3 Or

**How it was made:** I multiplied each bit with the bit corresponding to it using and gates and a 4 bit adder that I made.

**Not:**

 

Number of gates:

There are only 8 gates.


Detailed: 8 Not gates

How it was made:

The concept is pretty much simple already, just like the Move operation we have four inputs for operand 1 with four outputs being operand1 's complement, and four outputs are ground state's complements. E.g. 1111XXXX

↓      ↓  
Ground    Operand1 's complement

**And:**

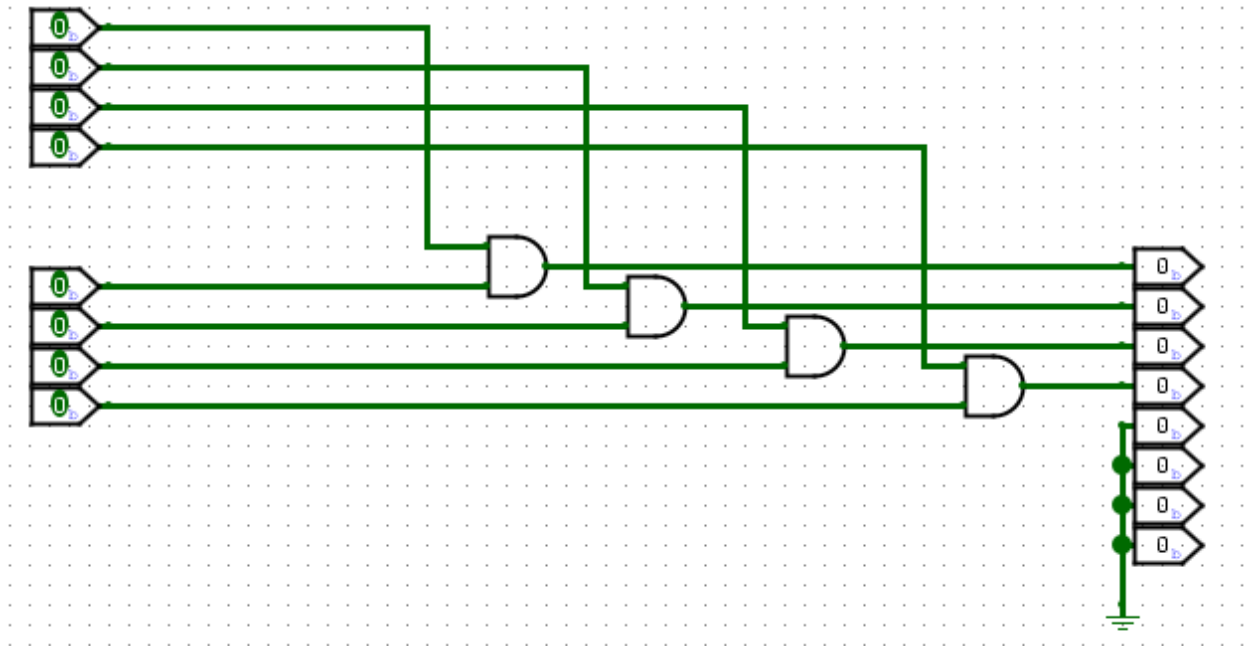


Number of gates:

Total: 4 Gates

Detailed: 4 And Gates

How it was made: every bit of each operand is compared to its opposite bit of the second operand by an And Gate

**Or:**

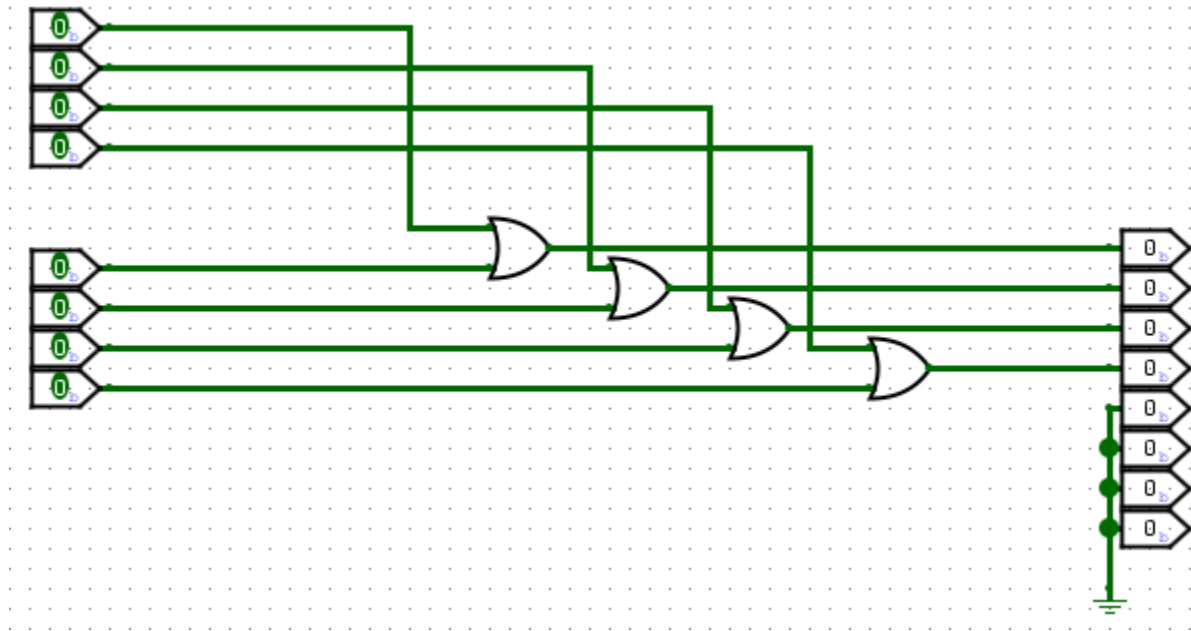

Number of gates:


Total: 4 Gates

Detailed: 4 Or Gates

How it was made: every bit of each operand is compared to its opposite bit of the second operand by an Or Gate

**Xor:**



 



Number of gates:

Total: 4 Gates

Detailed: 4 Xor Gates

How it was made: every bit of each operand is compared to its opposite bit of the second operand by Xor Gate

**Shift Right:**

  

Number of gates:



Total: 184 Gates

Detailed: 120 And Gates, 56 Or Gates, 8 Not Gates

How it was made: first I made a module that shifts the 8 bits of the input by only one bit to the right no gates were used in this module then I designed 2x1

multiplexer and then 8x1 multiplexer the first 4bit operand entered the module that shift 1bit and the output was entered to the shifting module 6 more times a row the output of each module was taken to be an input to the 8x1 multiplexer so it can be determined which shifting result should be taken according to the second operand readings

### **Shift Left:**

  

Number of gates:


Total: 184 Gates

Detailed: 120 And gates, 56 Or Gates, 8 Not Gates

How it was made: the same thing in the right shifting operation first I made a module that shifts the 8 bits of the input by only one bit to the left no gates were used in this module then I designed 2x1 multiplexer and then 8x1 multiplexer the first 4bit operand entered the module that shift 1bit and the output was entered to the shifting module 6 more times a row the output of each module was taken to be an input to the 8x1 multiplexer so it can be determined which shifting result should be taken according to the second operand readings

### **Main:**

L\_8\_bit\_16\_1\_MUX

 

Number of gates:


Total: There are a lot of gates inside this Giant, they sum up to a grand total of 480 gates, and that is not including the operation circuits.

Detailed:


The circuit consists of 240 And gates & 120 Or gates & 120 Not gates

How it was made:

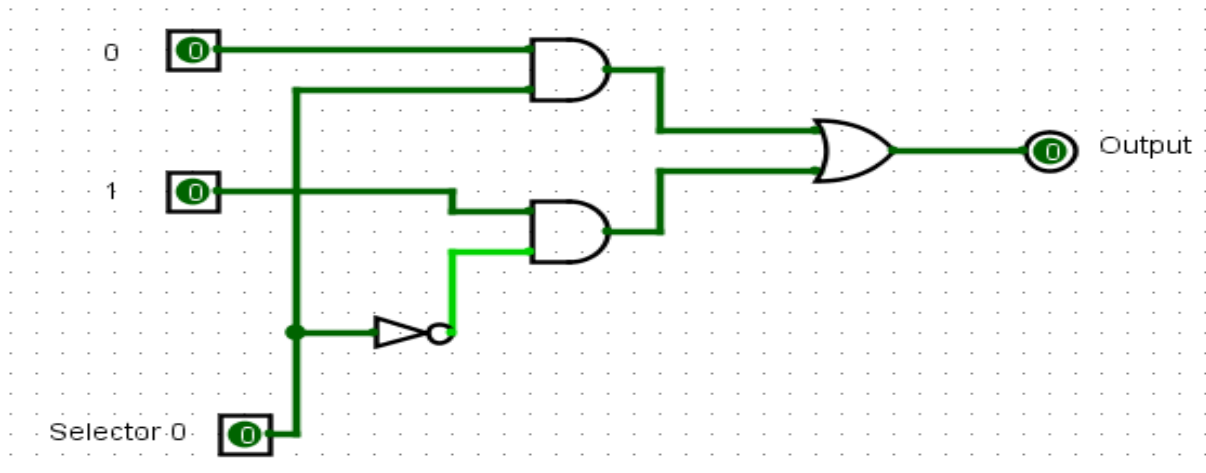
Because we are not allowed to use any gates other than the (Basic Gates: NOT, AND, OR, NAND, NOR, XOR, XNOR), We had to build the Multiplexers (MUX) from scratch starting with the 2\_1 MUX



Then the 4\_1 MUX

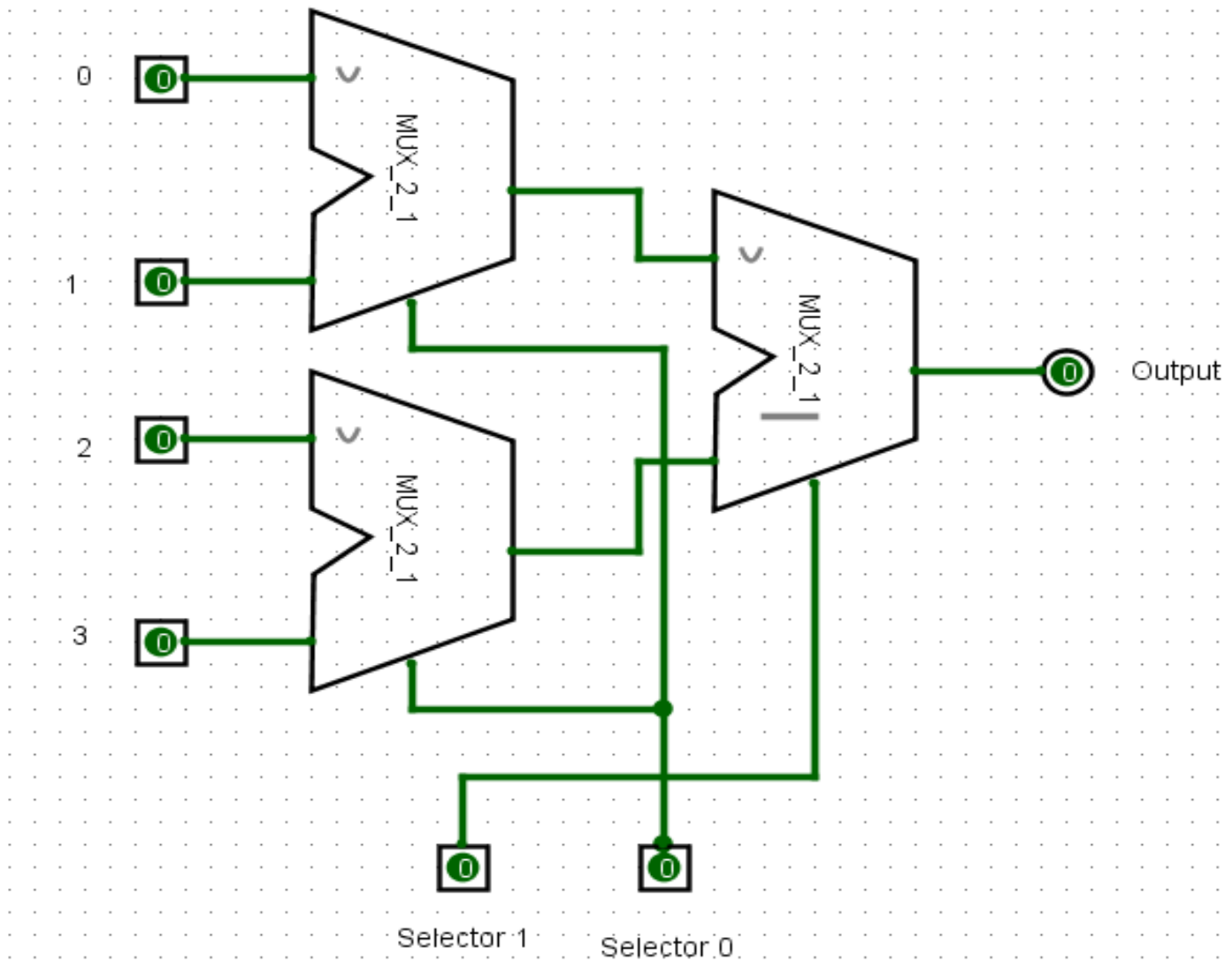


And the 8\_1 MUX

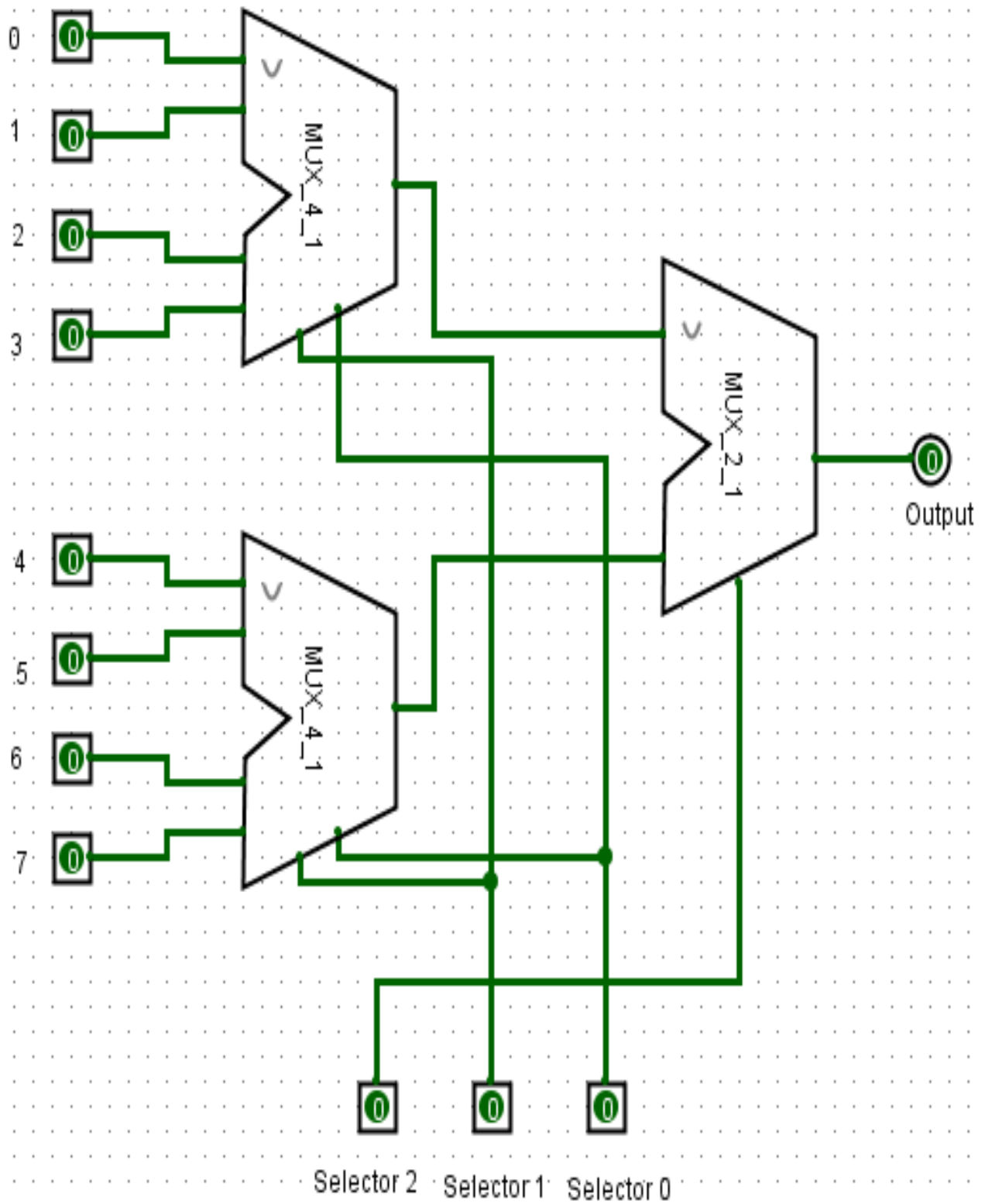

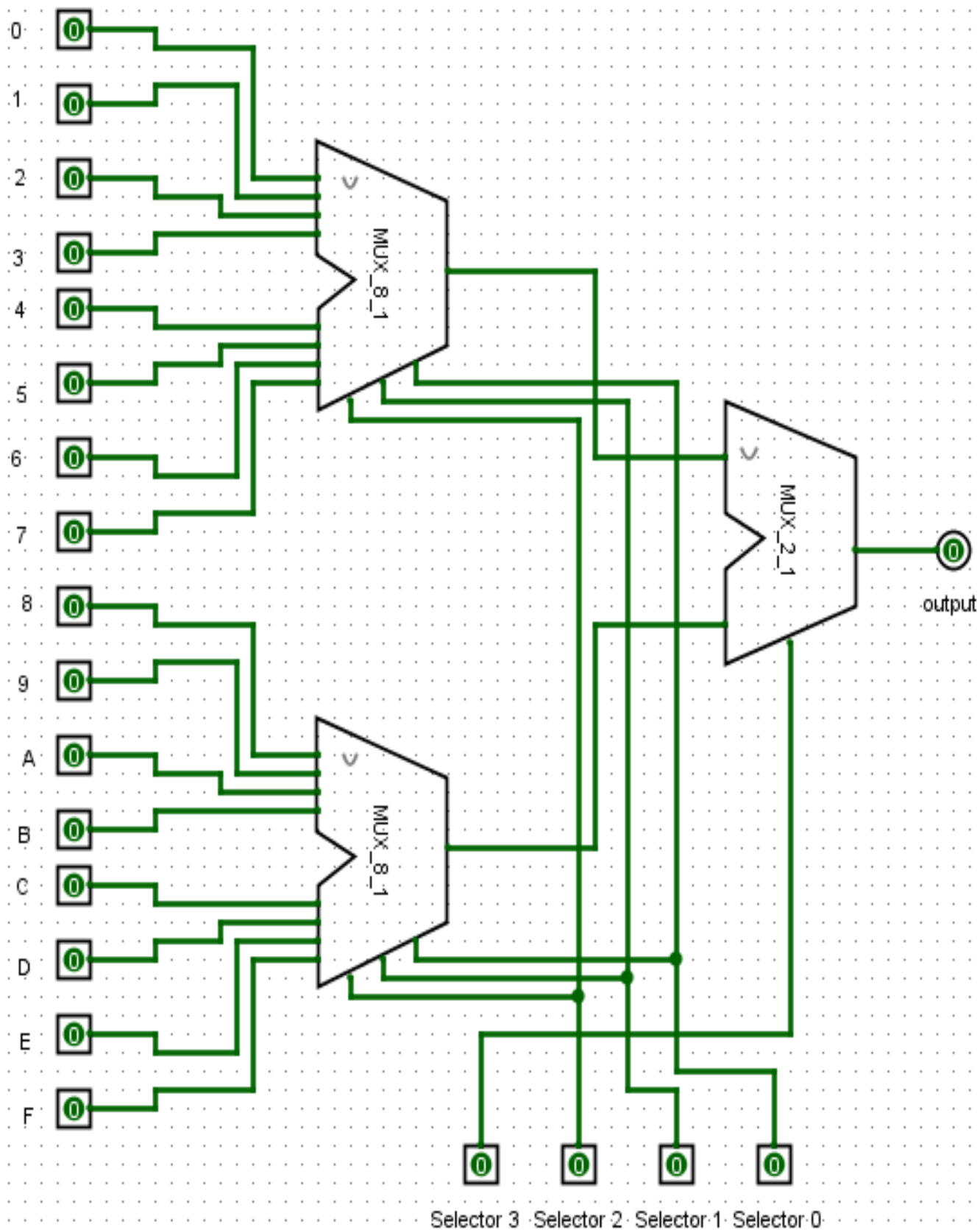Then Finally we have our 16\_1 MUX unit Used in the Main circuit of the ALU





After that we connected 8 (16\_1 MUX) to form the main circuit with a width of 8 bits.

By separating each element with the corresponding ones in the 8-bit 16\_1MUX circuit we connected each operation in place, and we are now done with our ALU unit.

